

# Solution (Basics 2. Sequential Logic)

## Problem 1

1) Flip-flop: changes on a clock edge


D flip-flop:

D	$D_{n-1}$	$D_n$	$D_{n+1}$	$D_n$	$Q_{n+1}$
Q	$Q_{n-1}$	$Q_n$	$Q_{n+1}$	0	0
CLK	$\uparrow n-1$	$\uparrow n$	$\uparrow n+1$	1	1

Analogy: think of a flip-flop as a device that changes the input into the output (dash.)

However, we should think of it as "what is going to be the next output given the current one?"

 Similarly:  $T \rightarrow Q_{n+1} = \bar{T}Q_n + T\bar{Q}_n$   
 $JK \rightarrow Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$





Before starting the problem, let's look a bit for the low hanging fruits:

-  $Z = B + X \rightarrow \triangle X$  is asynchronous!

- " $B_{n+1} = A_n$ " (B is ~~not~~ linked to the  $D_A$  flip-flop)

We can start the transition table now with these remarks (written in blue)

A	B	X	$D_A$	$D_B$	Z
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

Let's derive the equation for  $D_A$

Let's write the equation for all relevant gates

$$- E = \overline{BX}, F = \overline{X}, G = \overline{AX}, H = \overline{B\bar{X}A}, I = \overline{EHG}$$

$$\begin{aligned} \text{Then: } D_A = I = \overline{EHG} &= \overline{E} + \overline{H} + \overline{G} \\ &= \overline{\overline{BX}} + \overline{\overline{B\bar{X}A}} + \overline{\overline{AX}} \\ &= BX + B\bar{X}A + AX \end{aligned}$$

$$D_A = X(A+B) + AB\bar{X}$$

Then we can finalize the state transition table, written in purple.




## Problem 2 (cont.)
 
### 2) State Diagram

Our state is defined by A and B (current state)

It can be written 00, 01, 10, 11  $\rightarrow$  4 states



Let's build the transitions *in turquoise*

State 00  $A=0, B=0$ . Only variable, the input X.

- If  $X=0$ ;  $D_A=0, D_B=A=0$  and  $Z=B+X=0$
- If  $X=1$ ;  $D_A=0, D_B=0$  and  $Z=1$

Remark: the output depends on the state AND the input.  
It's a Mealy Machine!

State 01:  $A=0, B=1$ .

- If  $X=0$ ,  $D_A=0, D_B=0, Z=1$   
change of state!  $AB \neq D_A D_B$

- If  $X=1$ ,  $D_A=1, D_B=0, Z=1$

And similarly for the two other states

Sanity check: check that all states have two transitions  
(the input X takes  $2^1 = 2$  values)

### Interpretation

At clock tick  $n$ , we are in a state (e.g. 01)

Given an input, we can know the next state

AND the current output at the last clock tick







### Problem 3

Before we begin, let's look at the problem

We have a 3-input full adder, with carry output

4)


X	Y	Z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

First, the circuit is the sequential: it has

- 2 inputs X and Y
- A "current state" Z
- A "next state" C
- An output S

1) Just fill the truth table. It's just an adder

 2) The "current state" is Z  $\rightarrow$   $2^1$  states



3) Nearly: S depends on the state Z and the inputs X and Y

4)  $T_c \gg t_{pcq} + t_{pd} + t_{setup} = 2 + 4 + 2 = \boxed{8 \mu s} \leftrightarrow 125 \text{ MHz}$



Problem 4


1) For a JK flip-flop  $Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$   
 Or as a truth table, on a clock edge

J	K	$Q_n$	$Q_{n+1}$	
0	0	X	$Q_n$	Hold X = 0 or 1
0	1	X	0	Reset / Kill
1	0	X	1	Set / Setter
1	1	$Q_n$	$\bar{Q}_n$	Toggle

 2) Counter: something that counts (Juh)

↳ 2 bits: 0, 1, 2, 3  $\Leftrightarrow$  00, 01, 10, 11

Let's start with a "perfect" chronogram i.e. one that makes the function. Let  $a_1 a_0$  be the output of the counter




Observations -  $a_0$  toggles at each clock tick

-  $a_1$  toggles when  $a_0$  was 1 right before the clock tick.

$a_1^n$	$a_0^n$	$a_1^{n+1}$	$a_0^{n+1}$
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

Here the state is  $a_1 a_0$

 


We can assume there is a constant input



## Problem 4 (cont.)

We can propose the following schematic

 

## Problem 5

Before we begin, let's look at the problem overall. We need

- To count on 3-bits  $\rightarrow 0, 1, 2, \dots, 7$
- To count up or down: either  $0, 1, 2, \dots, 7$  or  $7, 6, 5, \dots, 0, 7, \dots$
- To have a reset, we would need to force the "next state" to be 0.

Note: The exercise was just written to have a reset in the circuit.

As it was not that interesting, we can get rid of it

1)

$a_2^n$	$a_1^n$	$a_0^n$	$u$	$a_2^{n+1}$	$a_1^{n+1}$	$a_0^{n+1}$
0	0	0	0	1	1	1
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	1	1
0	1	1	0	0	1	0
0	1	1	1	1	0	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	0
1	0	1	1	1	1	0
1	1	0	0	1	0	1
1	1	0	1	1	1	1
1	1	1	0	1	1	0
1	1	1	1	0	0	0



2) The state transition table gives the output directly for D-flip-flops

To use the D flip-flop of writing with  $D_n$  and  $Q_n$ , we have  $Q_{n+1} = D_n$ .

In the transition table,  $Q_{n+1} = a_i^{n+1}$  and  $Q_n = a_i^n$  ( $\forall i, 0 \leq i \leq 2$ )

By using K-maps, we will try to find the equation at the inputs of the flip-flops to encode the state transitions.

In our model, we have:

- 1 input:  $U$ : 1 if counting up, 0 if counting down
- 3 state variables:  $a_i$

$a_2 a_1 a_0$	00	01	11	10
00	1	0	1	0
01	0	0	1	1
11	0	1	0	1
10	0	0	1	1

$a_2^{n+1}$

$$a_2 a_2 \bar{a}_0$$

$$+ a_2 \bar{a}_1 U$$

$$+ a_2 a_0 \bar{U}$$

$$+ \bar{a}_2 \bar{a}_1 \bar{a}_0 \bar{U}$$

$$+ \bar{a}_2 a_1 a_0 U$$

$a_2 a_1 a_0$	00	01	11	10
00	1	0	0	1
01	0	1	1	0
11	1	0	0	1
10	0	1	1	0

$a_1^{n+1}$

$$\bar{a}_1 \bar{a}_0 U$$

$$+ a_1 \bar{a}_0 U$$

$$+ \bar{a}_1 a_0 U$$

$$+ a_1 a_0 \bar{U}$$

$a_2 a_1 a_0$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	0	0	0	0
10	0	0	0	0

$a_0^{n+1}$

$$= \bar{a}_0$$

3) Not difficult if you take an empty piece of paper




# Problem 6

74-393

As described, the 393 is a ripple counter.

 A ripple counter has a structure similar to the following



CLK

For a 4-bit counter the state-transition table is:

$a_3^n$	$a_2^n$	$a_1^n$	$a_0^n$	$a_3^{n+1}$	$a_2^{n+1}$	$a_1^{n+1}$	$a_0^{n+1}$
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	1	0	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	0	0	0



We can derive the equation for the counter by a method similar to problem 5.


But we can be smart!

- The LSB ( $a_0$ ) toggles on each clock tick.
- The second bit ( $a_1$ ) toggles when  $a_0$  is 1 and is going to 0
- The third bit ( $a_2$ ) toggles when  $a_1$  is 1
- The MSB toggles when  $a_2$  is 1 and is going to 0

Let's analyze this remark

- "From 1 to 0": falling-edge trigger
- "Toggling": T flip-flop

 The following is hence valid for falling-edge triggered flip-flop



If we wanted the rising-edge triggered version, we would just need to invert CLK



Problem 6 (cont.)

75-163

We can build a synchronous 5-bit counter with a simple "clock-through" method

- $a_0$  toggles on each clock tick
- $a_1$  should go to 1 or 0 when  $a_0$  is 1 in the current state.

In other words it toggles when  $a_0 = 1$

- $a_2$  will toggle when both  $a_0$  and  $a_1$  are 1
- $a_3$  —————  $a_2, a_1$  and  $a_0$  are 1s.

So


$$\left\{ \begin{aligned} a_0^{n+1} &= \overline{a_0^n} = \overline{a_0^n} \times 1 + 0 \times a_0^n \\ a_1^{n+1} &= \underbrace{a_0^n \overline{a_1^n}}_{\text{Toggling 1}} + \underbrace{\overline{a_0^n} a_1^n}_{\text{Hold if 0}} \end{aligned} \right.$$

$$a_2^{n+1} = \overline{a_2^n} (a_0 a_1) + a_2^n (\overline{a_0} + \overline{a_1})$$

$$a_3^{n+1} = \overline{a_3^n} (a_0 a_1 a_2) + a_3^n (\overline{a_0 a_1 a_2})$$

So with T flip-flops, of form  $Q_{n+1} = \overline{T} \overline{Q}_n + T Q_n$

we can derive the following circuit

 

No need to consider falling or rising edge here as the clock is not part of the values



1)	State Name	Member	Guest	Token	Exp	Next State	Open
	Idle	0	0	X	X	Idle	0
	Idle	0	1	X	X	Guest Enters	0
	Idle	1	0	X	X	Member enters	1
	Member Enters	0	0	X	0	Wait for Guest	0
	"	0	0	X	1	Idle	0
	"	0	1	X	0	Guest Follows	0
	"	0	1	X	1	Guest enters	0
	"	1	0	X	X	Member Enters	1
	Wait for guest	0	0	X	0	Wait for Guest	0
	"	0	0	X	1	Idle	0
	"	0	1	X	0	Guest Follows	0
	"	0	1	X	1	Guest Enters	0
	"	1	0	X	X	Member Enters	1
	Guest Follows	X	X	0	X	Guest follows	0
	"	X	X	1	X	Idle	0
	Guest Enters	X	X	0	X	Guest Enters	0
	"	X	X	1	X	Wait for Token 2	0
	Wait for Tk 2	X	X	0	X	Wait for Token 2	0
	"	X	X	1	X	Idle	1
	Illegal	1	1	X	X	Illegal	0

2) State can be encoded on 3 bits.


Which means Karnaugh Maps with 7 inputs is  $2^7$  cells long and tedious.

A good challenge though.



## Problem 7 (cont.)

3) It's a bit messy to draw...

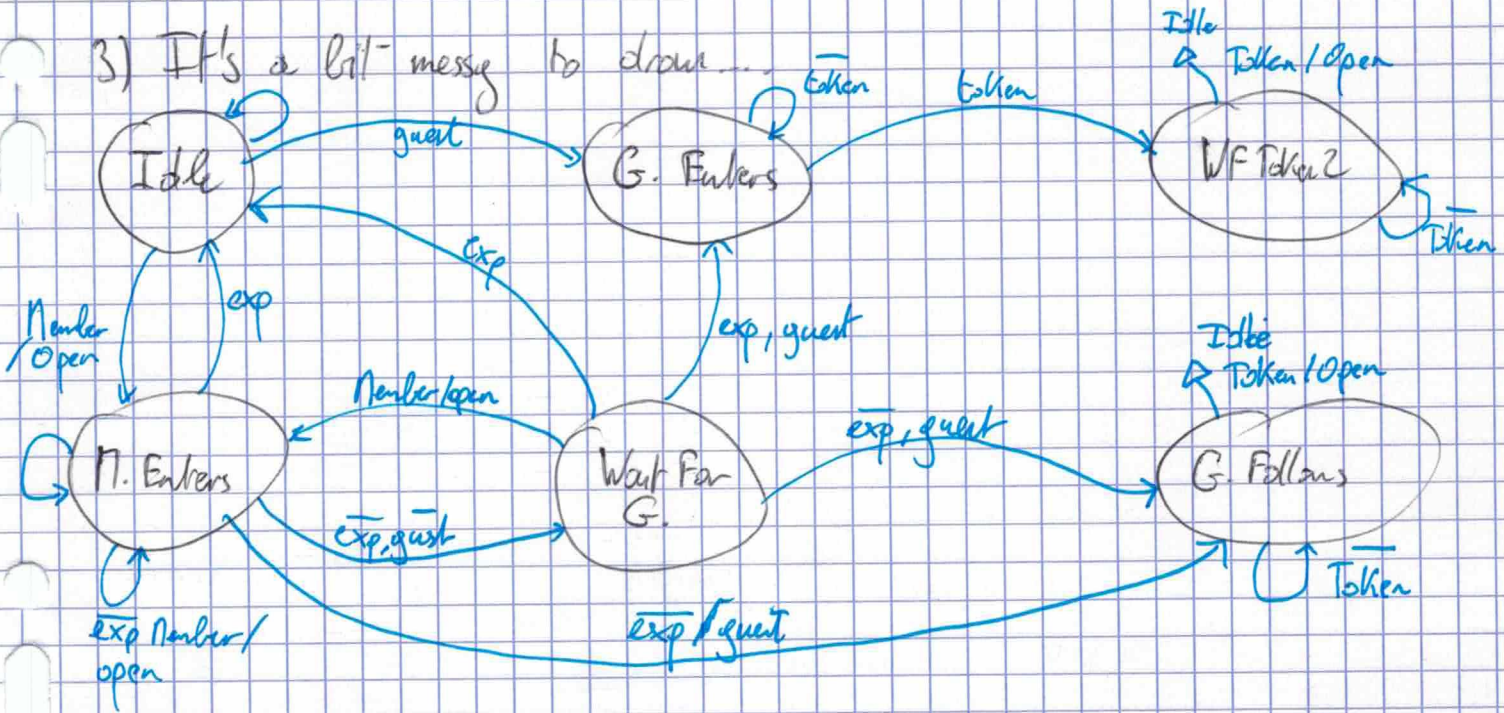

See the truth table for detailed transitions

In particular, the "closed barrier" output is not written. It's assumed to be there unless written otherwise

4) Output depends on state AND Inputs : it's a Mealy Machine.

---

END



